

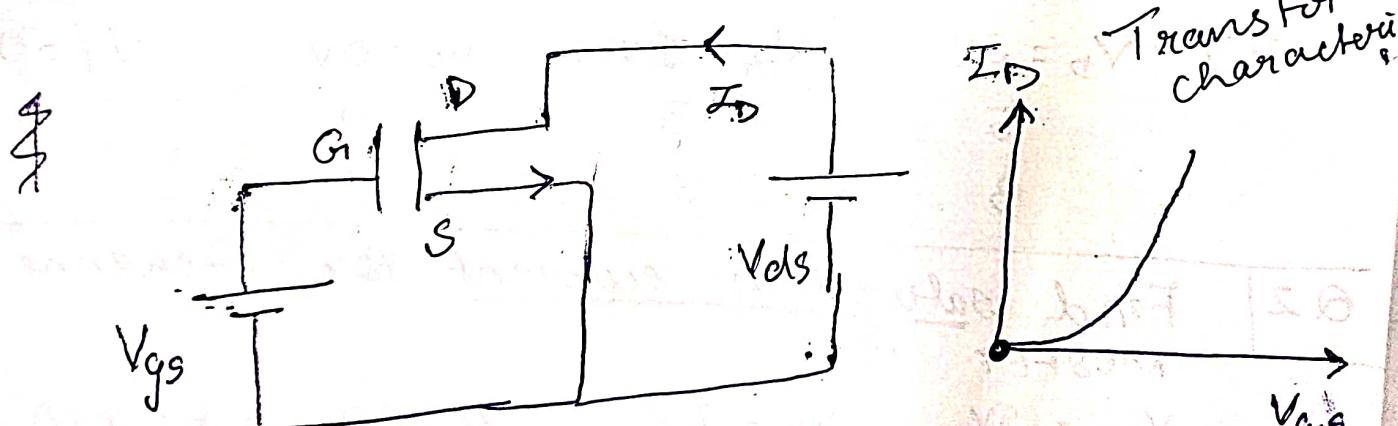


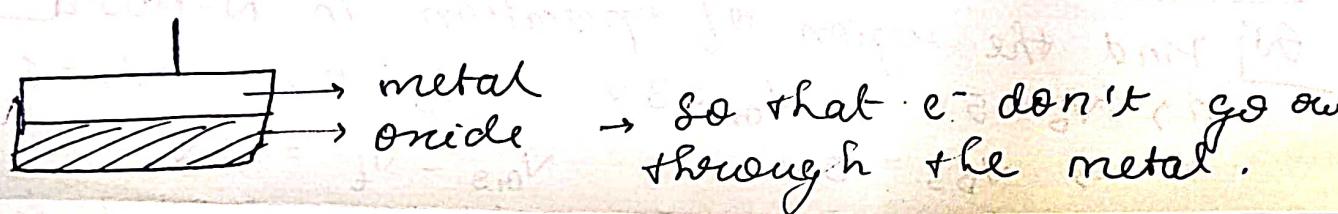Transistor: Transfer, resistor
Current flows without resistance
between collector & emitter.



$$V_{Or_1} < V_{Or_2} < V_{Or_3}$$

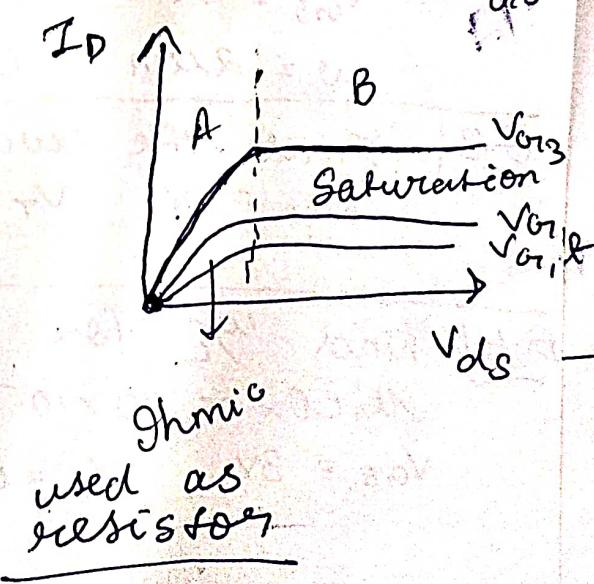

Function Transistor

Q1) IE

if $V_{ds} \geq V_{gs} - V_t$: Saturation

$V_{ds} < V_{gs} - V_t$: Linear

$$(in \text{ saturation}) I_D = \frac{K}{2} [V_{gs} - V_t]^2$$

$$K = \frac{\mu_n COx W}{L} \rightarrow \text{width}$$

$$(in \text{ linear}) I_D = \frac{K}{2} [2(V_{gs} - V_t)V_t - V_{ds}^2]$$

[Q1] Find the region of operation in N-MOSFET Tut 6

$$i) V_D = 5V \quad V_{G1} = 3V \quad V_S = 0V \quad V_T = 2V$$

$$\rightarrow V_{DS} = 5V \quad V_{G1S} - V_t = 2V$$

$$V_{G1S} = 3V \quad \therefore V_{DS} \gg V_{G1S} - V_t \therefore \text{Saturation}$$

$$ii) V_D = 3V \quad V_{G1} = 1V \quad V_S = 0V \quad V_T = 0.5V$$

$$\begin{array}{ccccccc} 5 & & 3 & & 1 & & 2 \\ | & & | & & | & & | \\ 3 & & 5 & & , & & 0 \end{array}$$

Q2] Find saturation current for n-channel MOSFET if

$$V_{G1S} = 5V \quad V_T = 2V \quad \mu_n COx = 89 \times 10^{-6}$$

$$W = 2\mu m \quad L = 1m$$

Q3] Find the current flowing through MOSFET

$$V_{G1} = 5V \quad V_T = 2V \quad V_{DS} = 2V \quad \frac{\mu_n COx W}{L} = 110 \times 10^{-6} A/V^2$$

Q4] Find $\frac{W}{L}$ for n-channel MOSFET whose

$$\mu_n COx = 110 \times 10^{-6} A/V^2 \quad \text{For an } I_D = 1mA,$$

$$V_{G1S} = 3V, \quad V_T = 0.5V$$

SV || 1K |

BJT | Bipolar Junction Transistor


11/10

TRANSFER + RESISTOR

BJT 1947




Not common current

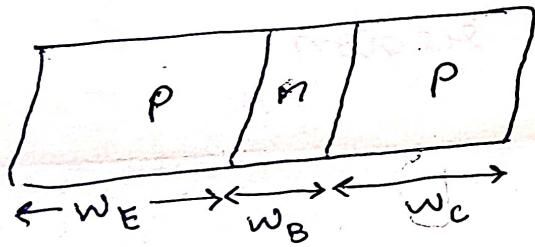

• Active Region -
Input : Forward
Output : Reverse

$$I_E = I_B + I_C$$

$$\alpha = \frac{I_C}{I_E}$$

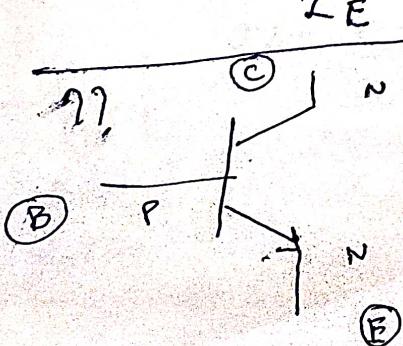

(UJT) FET

JFET


MOSFET

Enhancement

Depletion

$$w_E \approx w_C \gg w_B$$

Emitter Base Collector

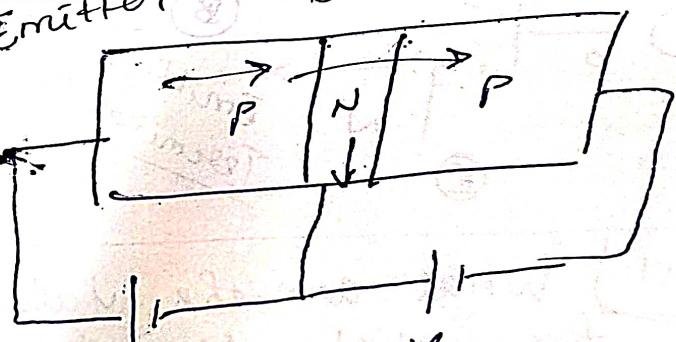

V_{EB}

$$I_C = \alpha I_B + I_{\text{leak}}$$

I_{CBO}

when input is open

V_{cc} $T = 10V$


Q1)

- Operation Regions :


Operation Region	Input I^n	Output I^n
Cut-off [DC]	Reverse	Forward / Reverse
Active	Forward	Reverse
Saturation [DC]	Forward	Reverse Forward

- All logic gates are operated in cut-off or saturation.

- For amplification, active region

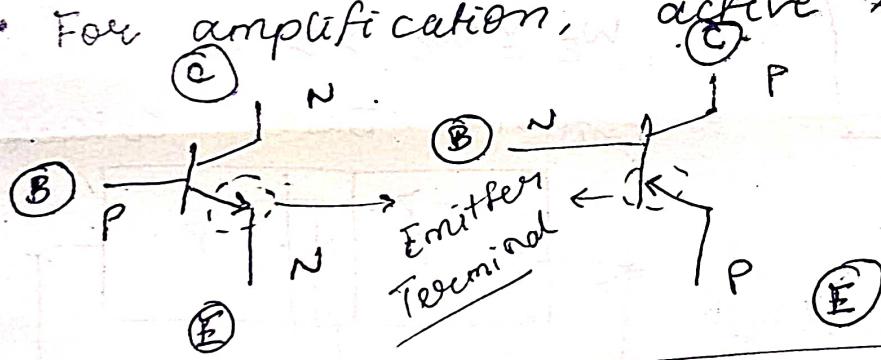

- Q1) What are the values of V_{BE} & V_{CB} for NPN transistor to be in an active region

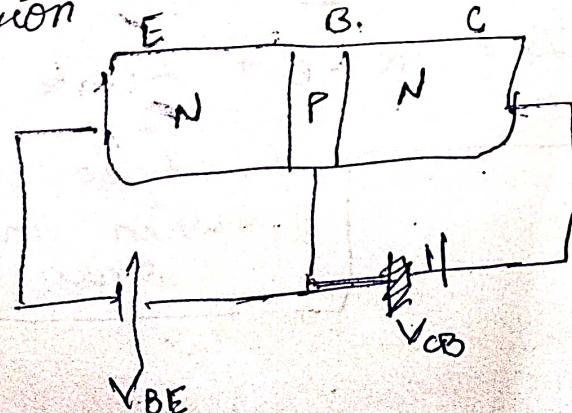
 $V_{BE} \rightarrow +ve$
 $V_{CB} \rightarrow +ve$

SV Q For PNP




$$E_{TMA} \propto 0.99$$

$$I_C = 0.99 \text{ mA}$$

$$I_B = I_E - I_C = 0.01 \text{ mA}$$



- Configurations

- CBC - Common Base config.

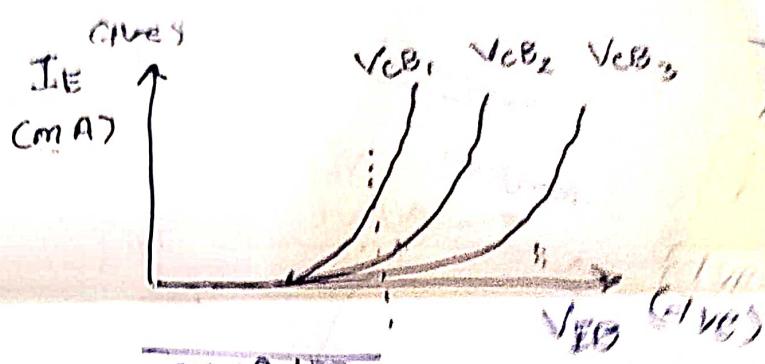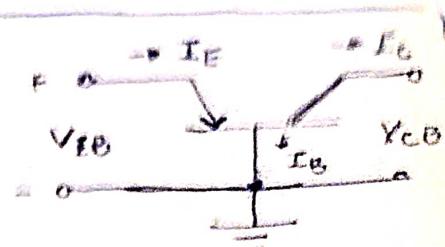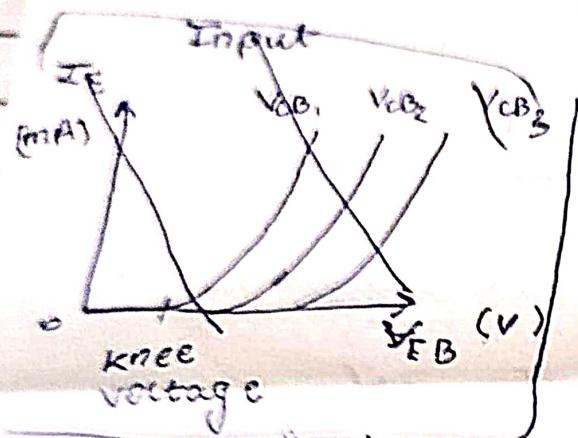



INPUT

I-V Characteristics
PNP CBC

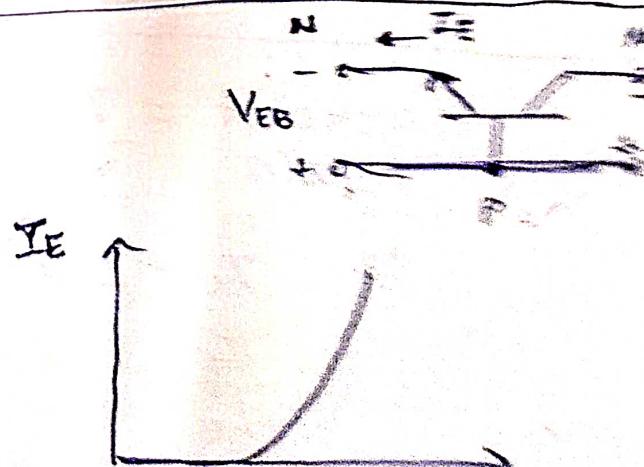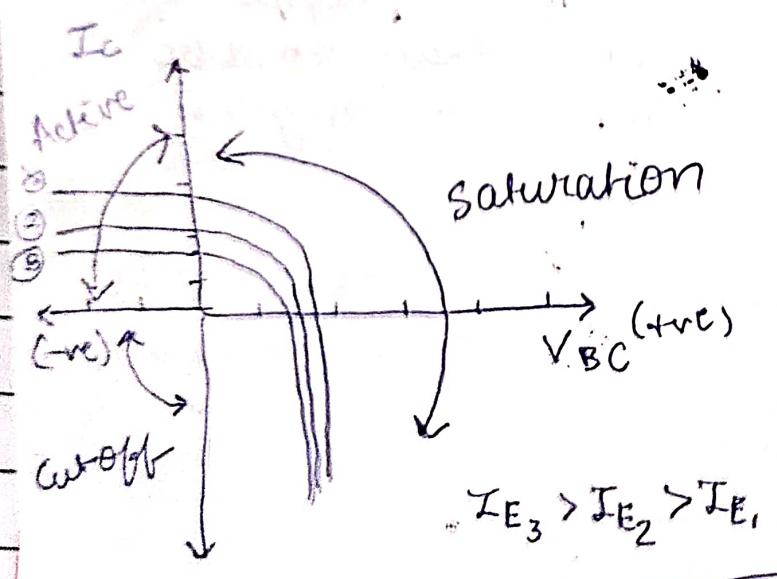


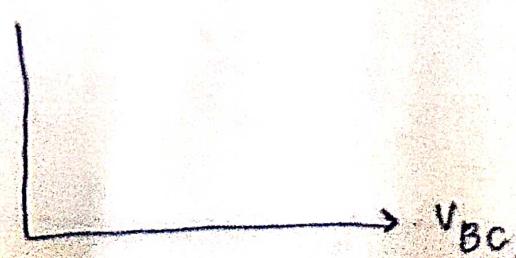BJT
RC \downarrow
Integrator
Differentiator



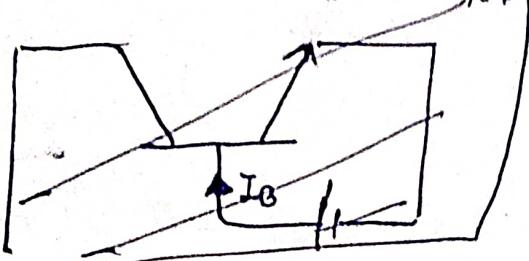


Input: forward
Output: reverse

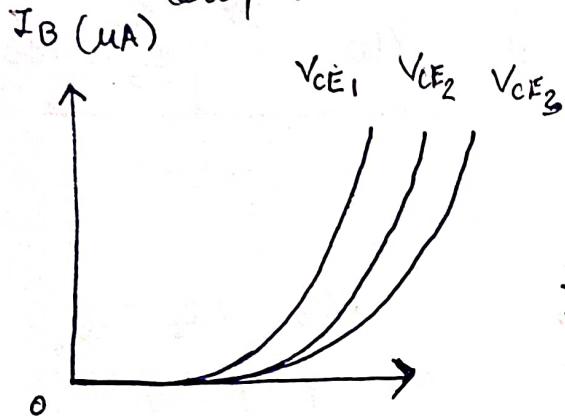

[Input voltage]

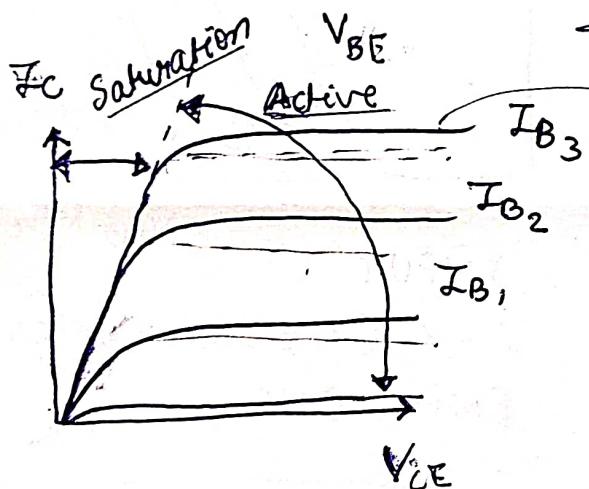Input Characteristics of NPN transistor in CEC



→ Not vertical but horizontal
 $I_{B_3} > I_{B_2} > I_{B_1}$

* Output is higher in CEC than in CBC in ACTIVE region

$$\text{Current gain} = \frac{I_{\text{out}}}{I_B} = \frac{I_C}{I_B}$$

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E + I_{CBO}$$

$$\Rightarrow I_C = I_C \alpha + I_B \alpha + I_{CBO}$$

$$\frac{I_C}{I_B} (1 - \alpha) = \alpha + \frac{I_{CBO}}{I_B}$$

$$\Rightarrow \boxed{\frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha} + \frac{1}{1 - \alpha} \cdot \frac{I_{CBO}}{I_B}}$$

$$\boxed{I_E = B + (1 + B) \frac{I_{CBO}}{I_B}}$$

$$\alpha = \frac{I_C}{I_E}$$

$$B - B\alpha = L$$

$$B = (\cancel{L})(1 + \beta)\alpha$$

$$\alpha = \frac{B}{1 + \beta}$$

$$1 + B = \frac{1}{1 - \alpha}$$

Leakage error is \rightarrow in CEC

(Q1) $I_E = 2\text{mA}$ $\alpha = 0.995$ reverse sat: $I = 100\text{nA}$
 at $T = 25^\circ\text{C}$ determine remaining current & ' B ' at
 75°C


$$\rightarrow I_{CBO} = 100\text{nA} \times \underbrace{2 \times 2 \times 2 \times 2 \times 2}_{5 \text{ times}} = 3200\text{nA}$$

$$25^\circ - 75^\circ = 5$$

$$I_C = 0.995(2\text{mA}) + 3.2\text{mA}$$

$$I_C = 1.99 + 0.0032 = 1.9932\text{ mA}$$
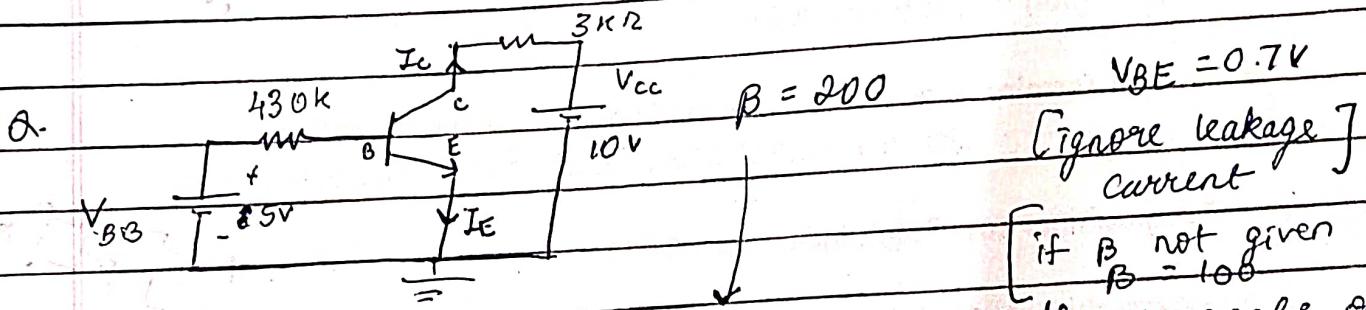
$$B = \frac{\alpha}{1-\alpha} = \frac{0.995}{1.995} = \frac{I_C}{I_B} = \frac{1.9932}{0.0068}$$



For a given Si transistor Determine all the currents of transistor & operating region. [if $V_{CE} = 0.2\text{V}$]

$$\rightarrow I_{BZ} \quad V_{BB} - I_B(430\text{k}\Omega) - V_{BE} = 0$$

$$I_B = \frac{5 - 0.7}{430\text{k}\Omega} = \frac{4.3}{4.3 \times 10^5} = 0.01\text{mA}$$

True $\rightarrow B = \frac{I_C}{I_B} = 200 \quad I_C = 2.01\text{mA}$


only in active region $\alpha = \frac{B}{1+B} = \frac{200}{201} \quad I_E = 2\text{mA} + 10\text{nA}$

$$V_{CC} - I_C R_C - V_{CE} = 0$$


$$V_{CC} - I_C R_C - V_{CE} = 0 \quad \text{from this if } V_{CE} > 0.2\text{V}$$

$$V_{CE} = 10 - 2\text{mA}(3\text{k}\Omega) = 4\text{V}$$

this active region

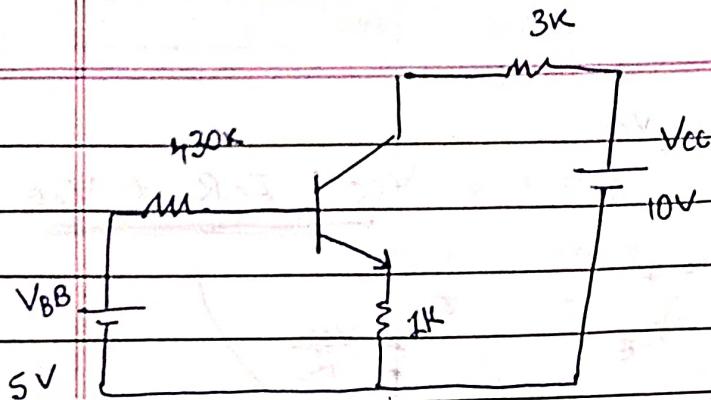

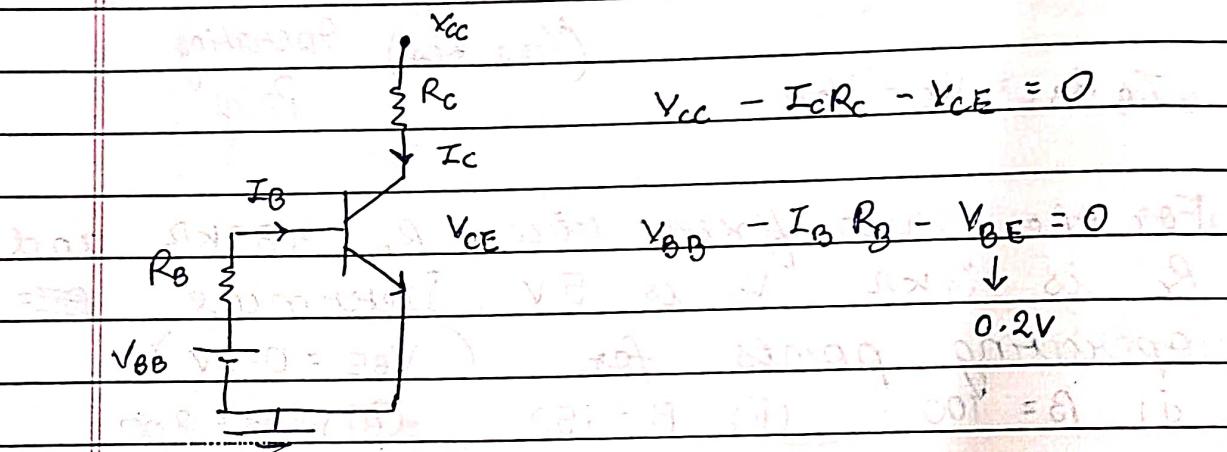
$$I_B = I_C \beta \quad \beta = \frac{I_C}{I_E} \quad [\text{in active region}]$$




$$I_B R_B + V_{BB} - I_C R_C - V_{CE} - I_{BE} R_E = 0$$

$$I_B R_B + V_{BB} - I_B R_B - V_{BE} = 0$$

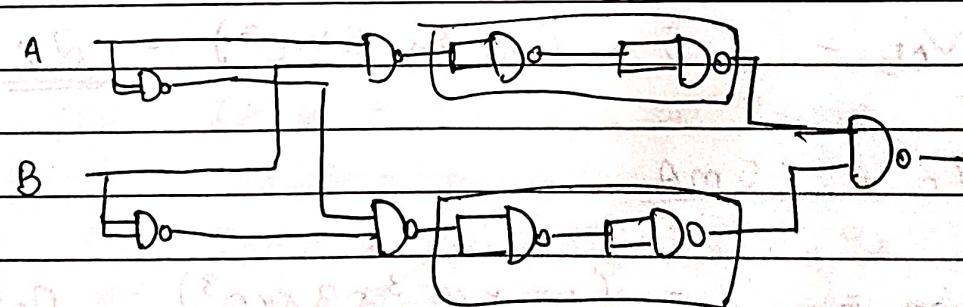In linear saturation region $I_E \approx I_C \quad \therefore \alpha \approx 1$



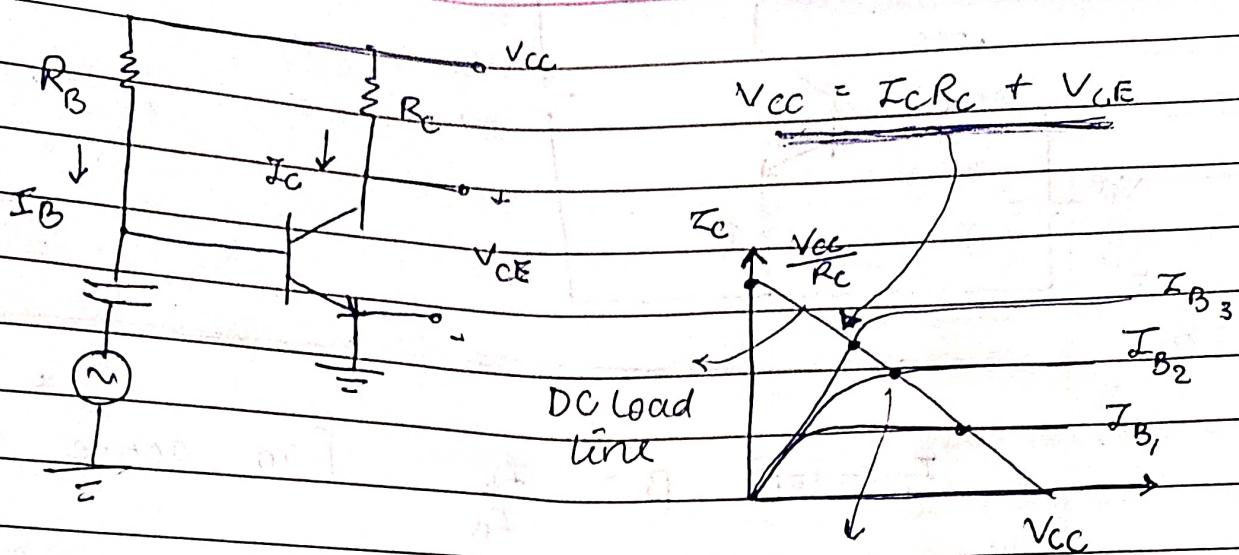

$$I_B R_B = V_{CC} - V_{BE}$$

(V_{CEQ}, I_{CQ}) Operating Point

For the given fixed bias, $R_B = 430\text{ k}\Omega$ and R_C is $3\text{ k}\Omega$, V_{CC} is 5 V . Determine operating points for ($V_{BE} = 0.7\text{ V}$)

- (i) $\beta = 100$ (ii) $\beta = 150$ (iii) $\beta = 200$

\rightarrow (i) $I_B = \frac{5 - 0.7 \times 10^{-3}}{430} = \frac{4.3 \times 10^{-3}}{430} = 10^{-5} \text{ A}$
 $= 0.01 \text{ mA}$

$$I_C = \beta I_B = \underline{1 \text{ mA}}$$

$$V_{CE} = 5 - (10^{-3} \times 3 \times 10^3) = \underline{2 \text{ V}}$$

(ii) $I_C = \underline{1.5 \text{ mA}}$

$$V_{CE} = 5 - (1.5 \times 10^{-3} \times 3 \times 10^3) = \underline{0.5 \text{ V}}$$

(iii) $I_C = \underline{2 \text{ mA}}$


$$V_{CE} = \underline{-1 \text{ V}} \quad [\text{Transistor in saturation}]$$

$$\therefore V_{CE} = 0.2 \text{ V}$$

$$V_{CE} = V_{CC} - I_C R_E$$

$$0.2 = 5 - I_C 3k\Omega$$
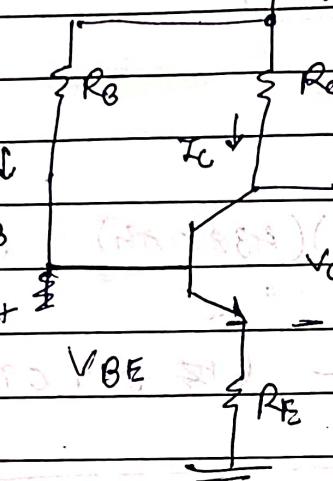
$$I_C = \frac{4.8 \times 10^{-3}}{3} = 1.6 \text{ mA}$$



SELF BIAS

- ↑ high cost

- ↑ Power losses

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E$$

$$(1+\beta) I_B$$

$$\Rightarrow I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta) R_E}$$

$$V_{CE} = V_{CC} - I_C (R_E + R_L)$$

~~$$Q: R_E = 2k\Omega, R_L = 1k\Omega, R_B = 430k\Omega, V_{CC} = 5V$$~~

~~$$\rightarrow i) \beta = 100$$~~

~~$$V_{CC} = I_C R_B + V_{BE} + (1+\beta) I_B R_E$$~~

~~$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$~~

~~$$V_{CC} = I_B R_B + V_{BE} + (1+\beta) R_E R_E$$~~

~~$$0 = I_C R_E - I_B R_B + V_{CC} - V_{BE}$$~~

~~$$\Rightarrow 0 = I_C R_E - I_B R_B + V_{CC} - I_C (R_E + R_L) = V_{BE}$$~~

~~$$0 = V_{CC} - I_B R_B$$~~

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$\Rightarrow V_{CC} - I_B R_B - V_{BE} - (1+\beta) I_B R_E = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (1+\beta) R_E}$$

$$I_B = 8.09 \times 10^{-6}$$


$$I_C = 8.09 \times 10^{-4}$$

$$V_{CE} = V_{CC} - (8.09 \times 10^{-4})(430 \times 10^3) = (101)(8.09 \times 10^{-6}) (1 \text{ k}\Omega)$$



$$= 8.09 \times 10^{-4} (347.87) - (8.09 \times 10^{-3})$$

$$\overline{A \cdot B} = (A+B) \cdot (\overline{A} + \overline{B}) = \overline{AB} + \overline{A} \overline{B}$$
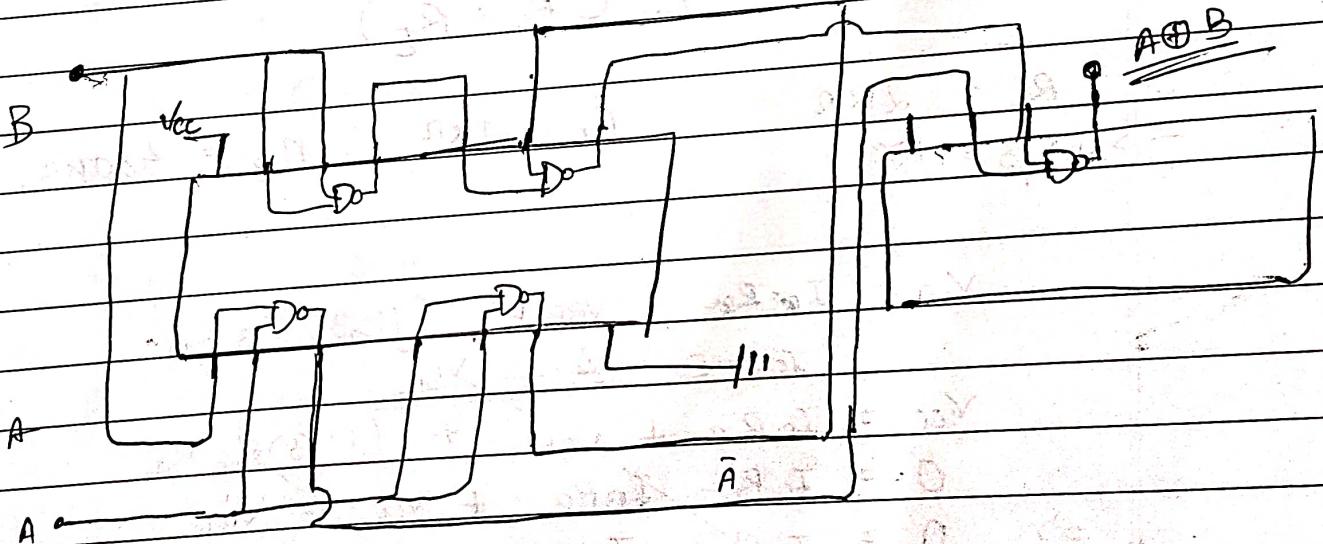
$$\begin{array}{l} \overline{A \cdot B} \\ (A+B) \end{array}$$



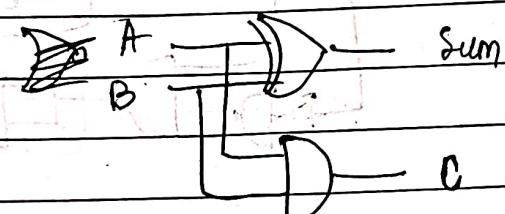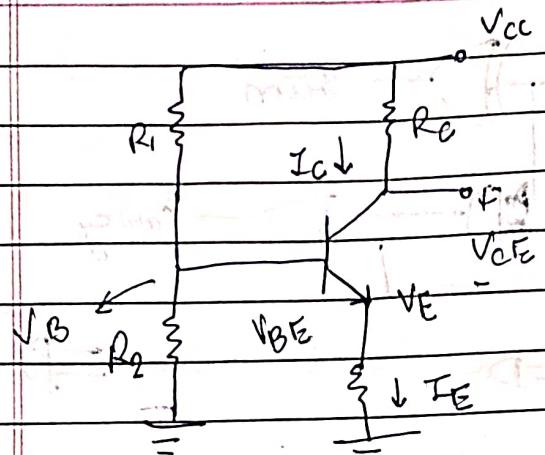
$$(A+B) \cdot (\overline{A} + \overline{B}) = A\overline{A} + A\overline{B}$$





$$A \cdot \bar{B} + \bar{A} \cdot \bar{B}$$

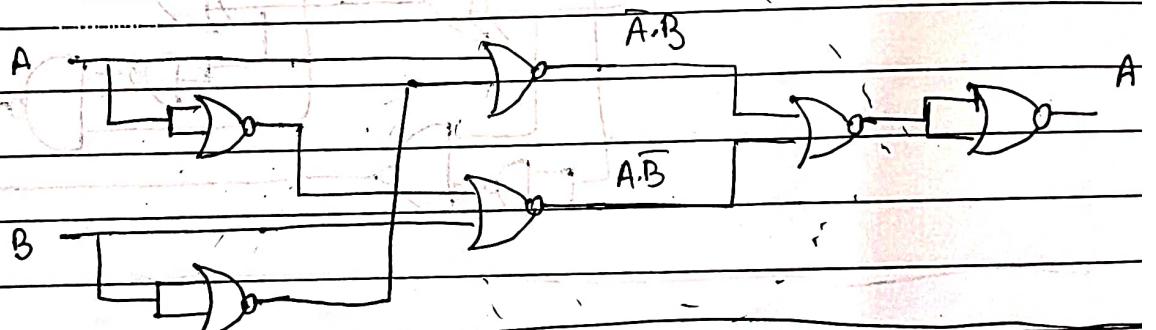
$$(A \cdot \bar{B}) + (\bar{A} \cdot \bar{B}) = A \cdot B + \bar{A} \cdot \bar{B}$$




$$(A+B)$$

$$\bar{A} \cdot B$$

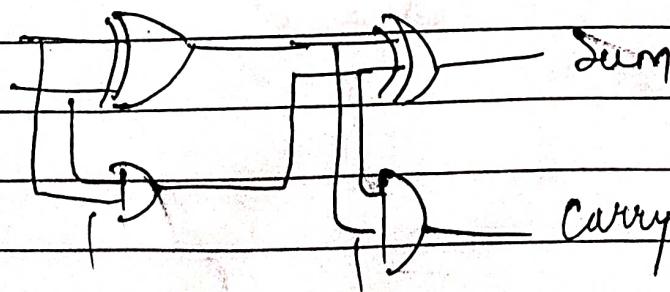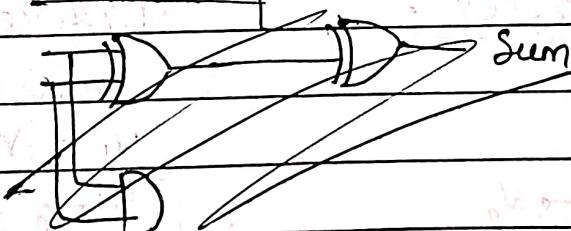

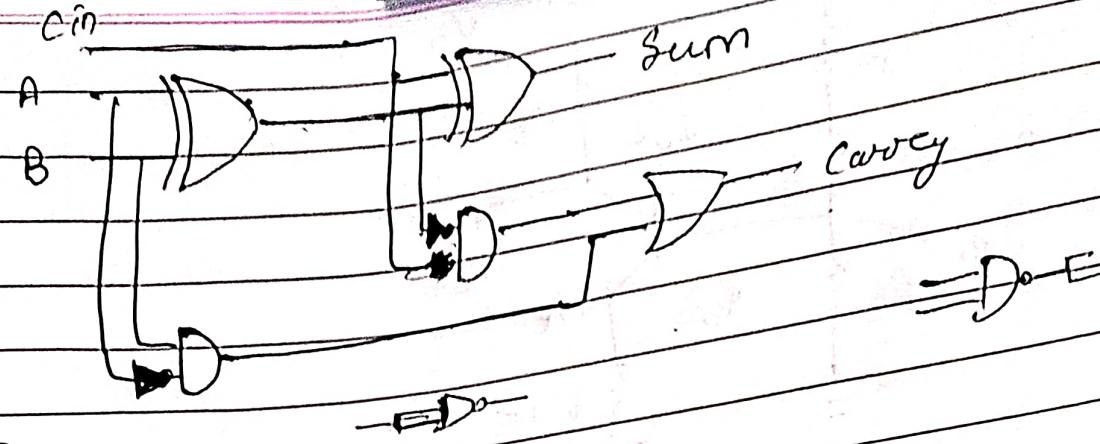


74153

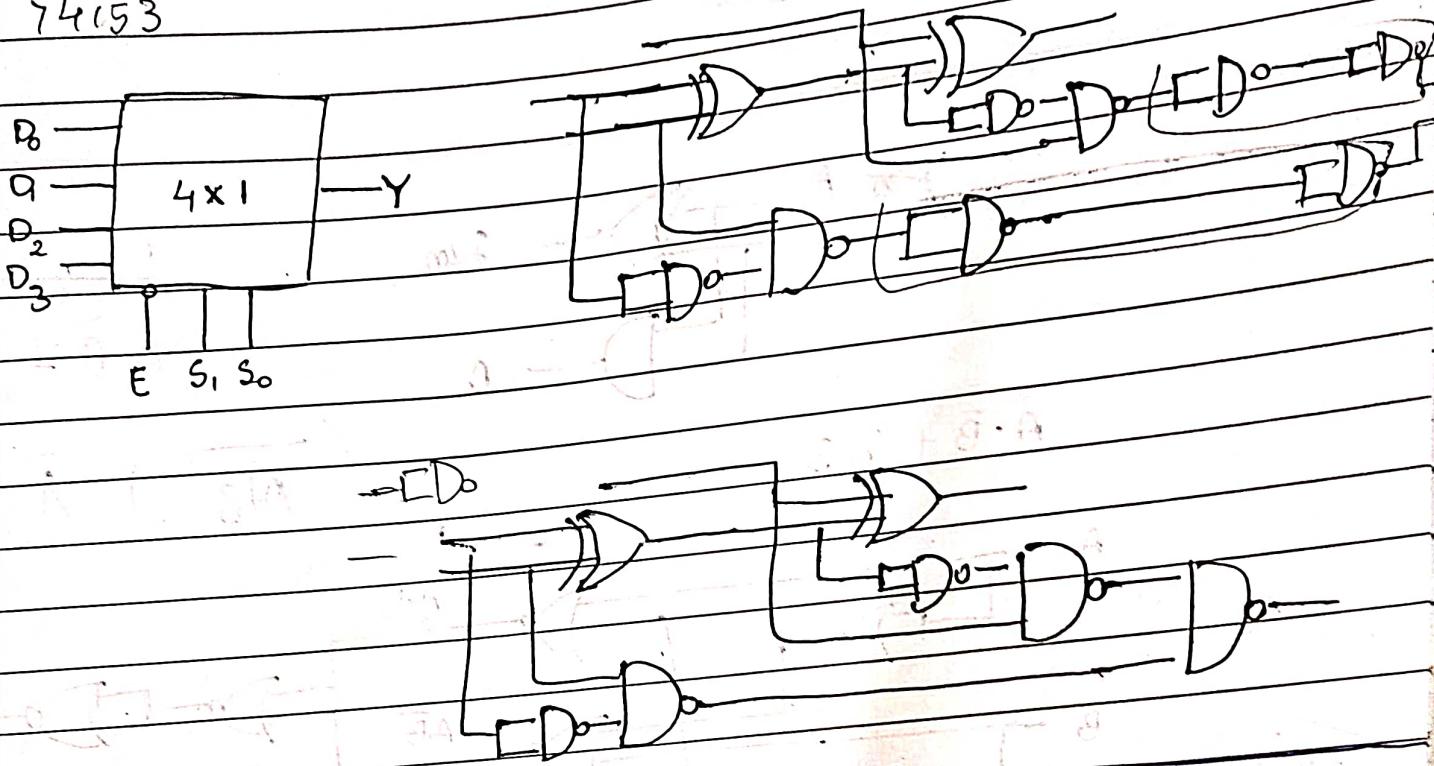


Operational Amplifier

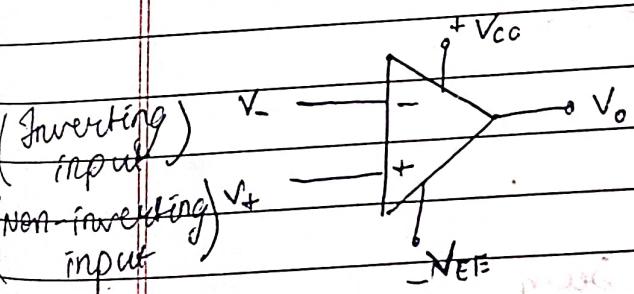Differential amplifier
(Noise cancellation)


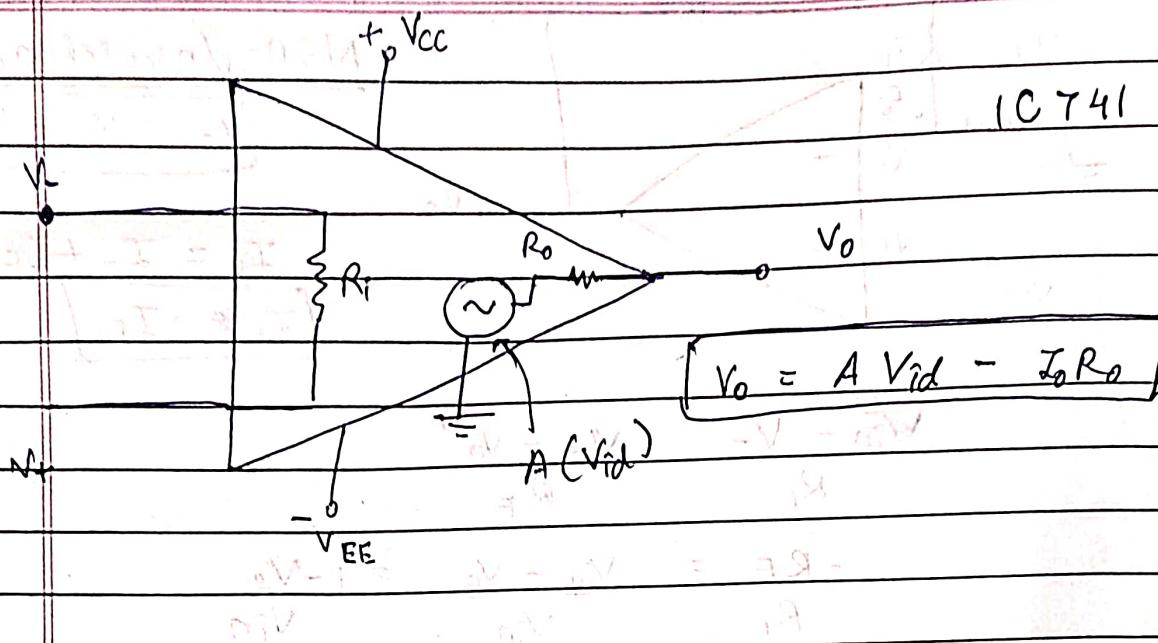
$$\begin{aligned} V_1 - V_2 \\ [V_1 + V_n] - (V_2 + V_n) \\ V_1 - V_2 \end{aligned}$$



Characteristics of Ideal OP Amp -


1. R_i tends to infinite (in M^2 order)
2. R_o tends to zero ($\approx \infty$)
3. Open loop gain A is ∞ [2×10^5]

Conclusion -

$$1) A I_F = I_- = 0$$


$$2) V_o = A V_id$$
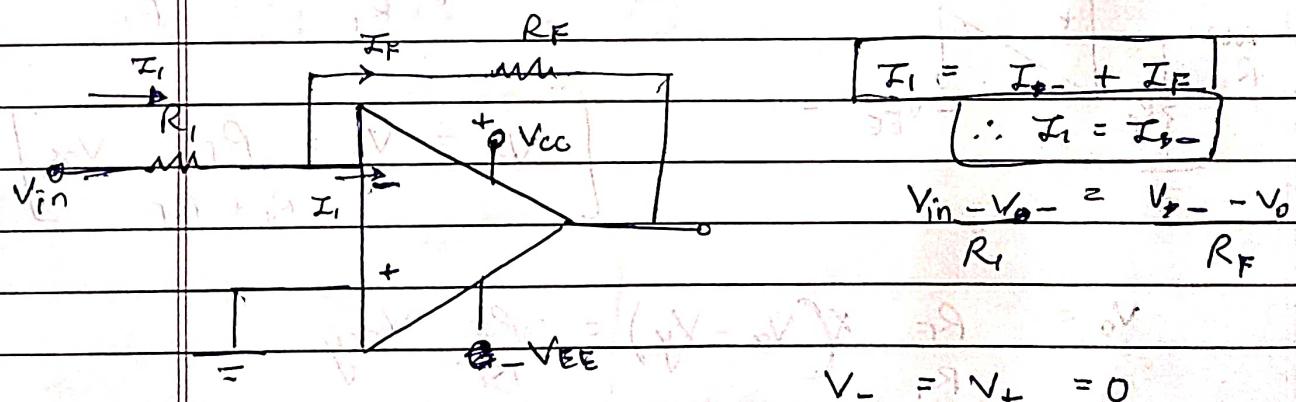
$$3) V_+ = V_- = -V_{EE} \quad [\because A \rightarrow \infty]$$



$$V_o = A F V_in = -R_F / R_i V_in$$

Inverting
Amplifier

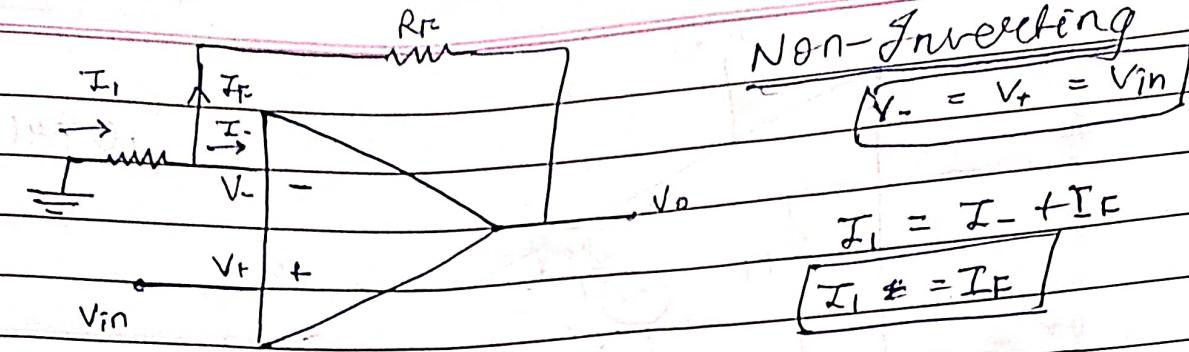

Non-Inverting

$$V_- = V_+ = V_{in}$$

$$I_i = I_- + I_F$$

$$I_i \neq I_F$$


$$\frac{V_o}{R_F} - V_- = V_- - V_o$$

$$R_i \quad R_F$$

$$-\frac{R_F}{R_i} = \frac{V_{in} - V_o}{V_{in}} = 1 - \frac{V_o}{V_{in}}$$

$$-\frac{1 + R_F}{R_i} = \frac{V_o}{V_{in}}$$

Differential Amplifier

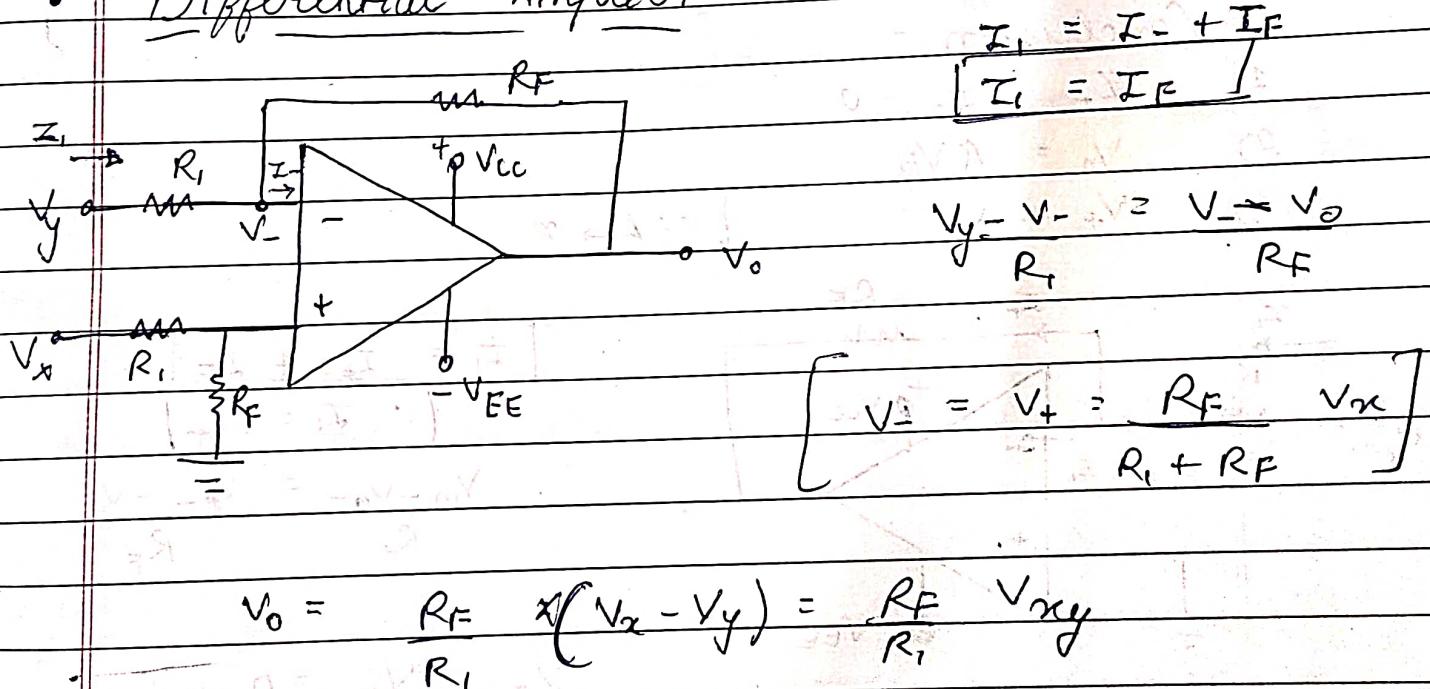

$$I_i = I_- + I_F$$


$$I_i = I_F$$

$$V_y = V_- = V_+ = V_o$$

$$V_z = V_+ = \frac{R_F}{R_i + R_F} V_x$$

$$V_o = \frac{R_F}{R_i} (V_x - V_y) = \frac{R_F}{R_i} V_{xy}$$

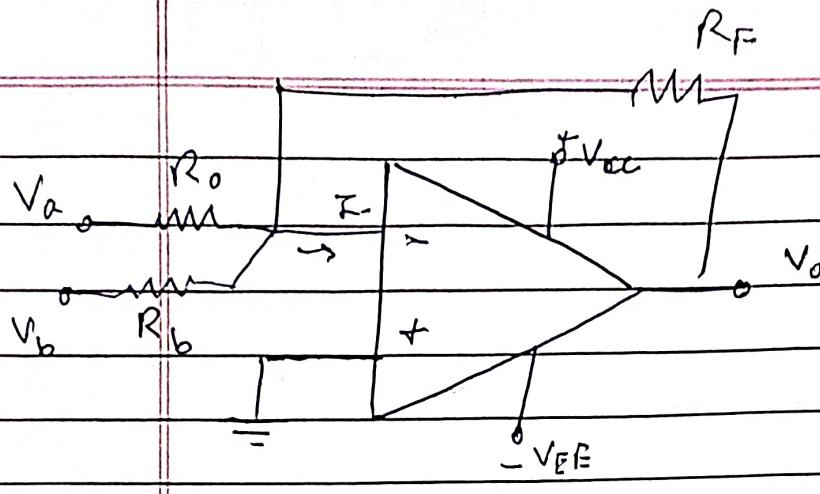If all resistors are same then $V_o = V_x - V_y$



$$\frac{V_a}{R_a} + \frac{V_b}{R_b} = \frac{-V_o}{R_F}$$

$$V_o = - \left[\frac{R_F V_a}{R_a} + \frac{V_b R_F}{R_b} \right]$$

Case I :

$$R_F = R_a = 2R_b$$

$V_o = - (V_a + 2V_b)$ Scaling Ampiffer


Case II :

$$R_F = R_a = R_b$$

$\therefore V_o = - (V_a + V_b)$ Summing circuit +

Case III : $2R_F = R_a = R_b$

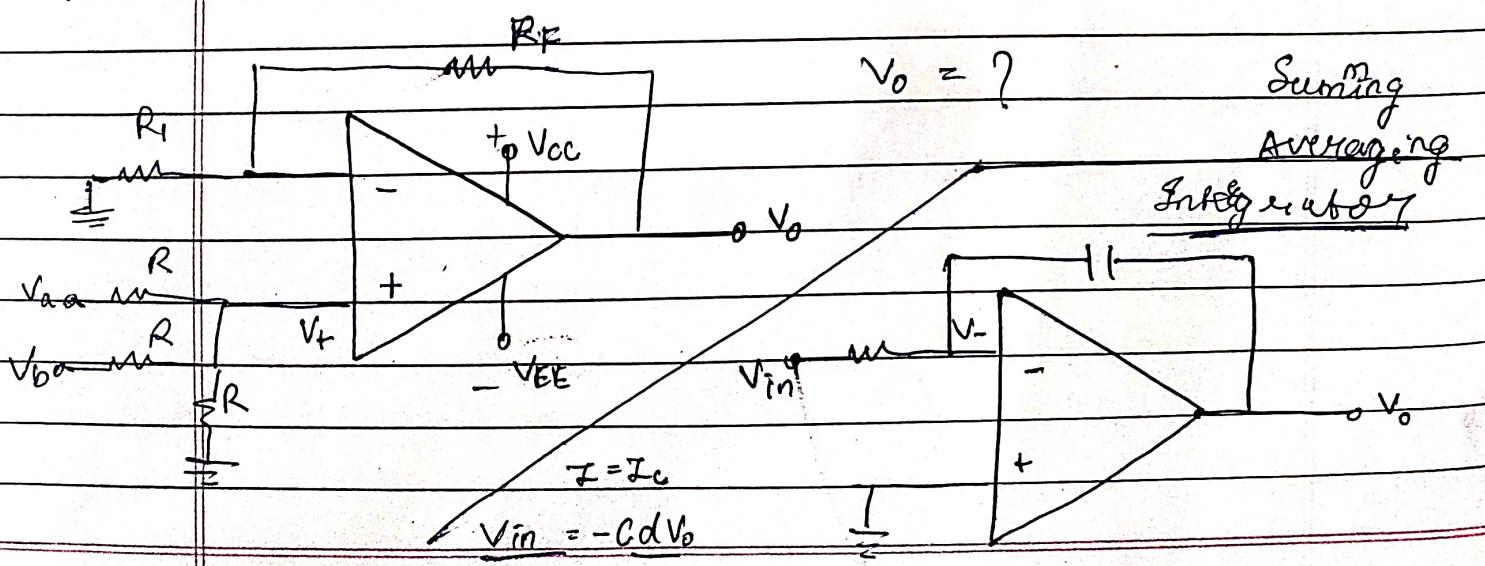$\therefore V_o = - \left(\frac{V_a + V_b}{2} \right)$ Averaging



$$N_o = \frac{1}{RC} \int V_{in} dt$$

Interchange
R & C