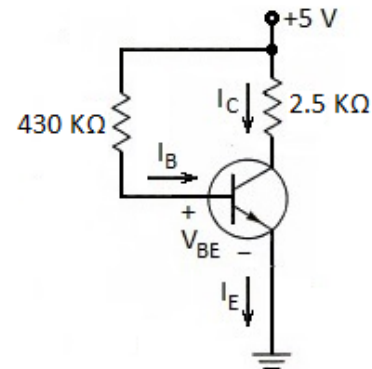


## TUTORIAL-IX


SEM-III, B.Tech(Computer Engineering), SVNIT, Surat

### Topic: BJT biasing and MOSFET


- 1) For the circuit shown in below figure, if  $V_{BE} = 0.7$  V, then determine the dc voltage at the collector for  $\beta = 100, 150$  and  $200$ . Comment on the results.



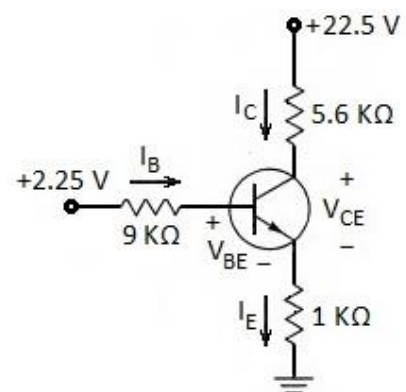- 2) Determine the operating point of silicon transistor circuit shown in below figure for  $\beta = 100, 150$  and  $200$ . Comment on the results.



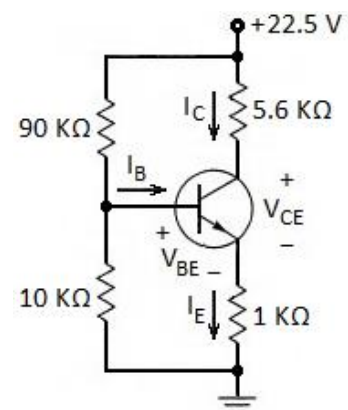- 3) A silicon transistor is used in circuit given in figure. Calculate the operation point for this transistor circuit for  $\beta = 100$  and  $\beta = 200$ . Comment on the results.



- 4) Design a voltage-divider biasing circuit to fix the operating point at (6 V, 4 mA) for the silicon BJT with  $\beta = 200$ , operating at 12 V supply.
- 5) In the given circuit, the n-channel MOS device has  $K$  is 1.67 milli-siemens per volt, and  $V_T$  is 0.5 volts. In the circuit  $R_1 = 635.3$  kΩ and  $R_2 = 100$  kΩ. What is the maximum value of  $R_D$  for which the device is in saturation?

